

How to Calibrate 10X Probe

How 10X Probe Works

Standard oscilloscope probe has a switch on its handle (see Fig. 1 below) which can select probe attenuation between 1X and 10X. By placing the switch at 10X position what it actually does is putting a 9M ohm resistor (R_a) in series with oscilloscope input, as shown in the schematic of Fig. 2. Since typical oscilloscope has input resistor (R_s) of 1M ohm the 9M resistor R_a and oscilloscope input impedance form a 1/10 divider. This divider delivers 1/10 of input voltage to oscilloscope.

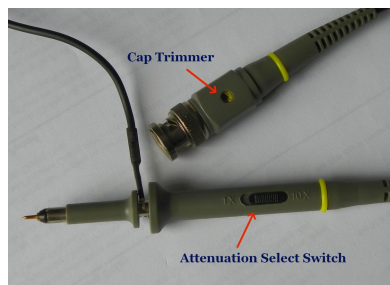


Fig. 1

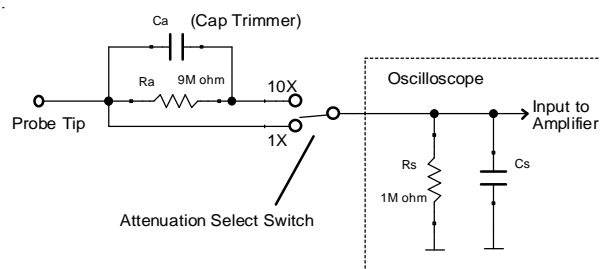


Fig. 2

Why Calibration of 10X Probe Is Required

As you may know oscilloscopes always have some kind of input capacitance (C_s). R_a and C_s act as a low-pass filter. This low-pass filter could significantly impact oscilloscope performance for signals that have high frequency components because they get larger attenuation here. As a result what we see on oscilloscope screen is not the real signal but a distorted one.

Obviously this problem is caused by C_s . To de-effect C_s we can add another capacitor C_a in parallel with R_a so as to "compensate" losses caused by C_s . With C_a in place higher frequency components can bypass through it and result in less attenuation. We can reasonably expect that C_a will improve 10X probe performance. But what value of C_a should be? We know that in order to keep signal original we should ensure all frequency components are equally maintained in given bandwidth. Mathematics can prove that for the circuit in Fig. 2 all frequency components are equally passed when the following equation holds.

$$C_a/C_s = R_s/R_a$$

Since R_s , R_a , and C_s are determined we can use a trimmer as C_a (see Fig. 1) and tune it so that the above requirement is met.

How To Calibrate 10X Probe

To calibrate 10X probe (tuning C_a) we need a good quality square signal source. The reason for choosing square signal is that it contains rich frequency components and is easy to generate. There is no strict requirements for its frequency and amplitude. Frequency from several hundred Hz to several KHz and amplitude from less than 1 volt to several volts are acceptable. But most importantly the waveform shape must be good. It should have nice and sharp right angles at its corners. When you have the signal ready follow the steps listed below to complete the calibration.

1. Connect probe to signal source. Select 10X attenuation by placing the switch at 10X position.

2. Change oscilloscope settings so that 1 ~ 2 cycles are displayed on screen with amplitude being 2 ~ 3 divisions. (see Fig. 3 as an example)
3. Turn Ca with a small screw driver so that best waveform shape (the middle of Fig. 3) is obtained.

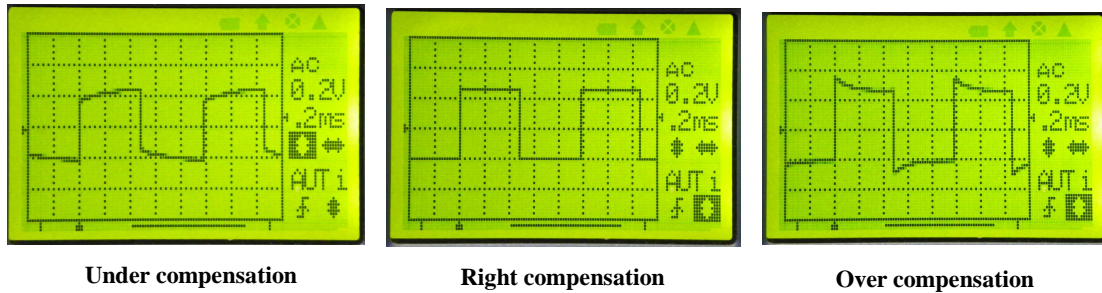


Fig. 3

Why we know the calibration is done when good square waveform is obtained?

From signal theory we know that square signal consists of many different frequency components. When it passes a circuit if some components loss (or gain) more than others we will see its shape distorted at output. Reversely, if we see a perfect waveform is obtained at output we know that all frequency components are maintained.

(zliu)

Revision History

Version	Date	Descriptions
01	2012.05.23	First draft